


Question

1 2 3 4 5 6 7 8 9 10

1. Question Details

SerCP8 16.P.044. [882184]

Find the equivalent capacitance between points a and b in the combination of capacitors shown in the figure below. ($C_1 = 3.0 \mu\text{F}$ and $C_2 = 4.0 \mu\text{F}$.)

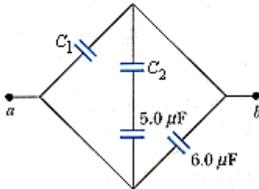 μF


2. Question Details

SerCP8 17.P.008. [1716982]

An aluminum wire carrying a current of 2.0 A has a cross-sectional area of $7.0 \times 10^{-6} \text{ m}^2$. Find the drift speed of the electrons in the wire. The density of aluminum is 2.7 g/cm^3 . (Assume three electrons are supplied by each atom.)

 m/s

3. Question Details

SerCP8 17.P.028. [882434]

A wire 3.00 m long and 0.450 mm^2 in cross-sectional area has a resistance of 41Ω at 20°C . If its resistance increases to 41.3Ω at 28.0°C , what is the temperature coefficient of resistivity?

 $^\circ\text{C}^{-1}$

4. Question Details

SerCP8 17.P.034. [882451]

If electrical energy costs 12 cents, or $\$0.12$, per kilowatt-hour, then what would the following events cost?

(a) burning a 100 W light bulb for 24 h straight

$\$$

(b) operating an electric oven for 3.0 h if it carries a current of 20.0 A at 220 V

$\$$

5. Question Details

SerCP8 17.P.042. [882418]

Batteries are rated in terms of ampere-hours ($\text{A} \cdot \text{h}$). For example, a battery that can produce a current of 3.00 A for 5.00 h is rated at $15.00 \text{ A} \cdot \text{h}$.

(a) What is the total energy stored in a 12.0-V battery rated at $54.0 \text{ A} \cdot \text{h}$?

kWh

(b) At $\$0.0660$ per kilowatt-hour, what is the value of the electricity produced by this battery? NOTE: Enter your response with hundredths precision.

¢

The cost of electricity varies widely throughout the United States; \$0.120/kWh is a typical value. At this unit price, calculate the cost that would result from each of the following:

(a) leaving a 40.0 W porch light on for 2 weeks while you are on vacation

\$

(b) Making a piece of dark toast in 3.00 min with a 1000 W toaster.

\$

(c) drying a load of clothes in 40.0 min in a 6000 W dryer

\$

(a) Find the equivalent resistance between points a and b in the figure below ($R = 10.0 \Omega$).

Ω


(b) A potential difference of 34.0 V is applied between points a and b . Calculate the current in each resistor.

I (4.00 Ω) = A


I (7.00 Ω) = A

I (10.0 Ω) = A

I (9.00 Ω) = A

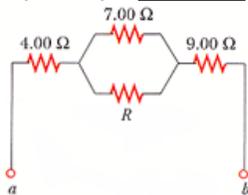

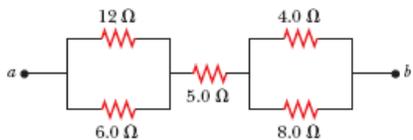Consider the combination of resistors shown in the figure below.



(a) Find the equivalent resistance between point a and b .

Ω

(b) If a voltage of 48.5 V is applied between points a and b , find the current in each resistor.

12 Ω A


6 Ω A

5 Ω A

4 Ω A

8 Ω A

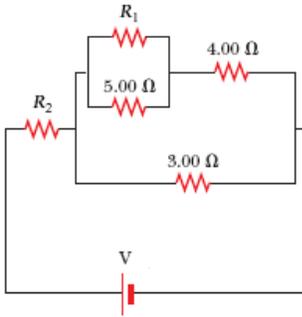Consider the circuit shown in the figure below. Use the following as necessary: $R_1 = 8.00 \, \Omega$, $R_2 = 2.30 \, \Omega$, and $V = 7.00 \, \text{V}$.



(a) Calculate the equivalent resistance of the R_1 and $5.00 \, \Omega$ resistors connected in parallel.

 Ω

(b) Using the result of part (a), calculate the combined resistance of the R_1 , $5.00 \, \Omega$, and $4.00 \, \Omega$ resistors.

 Ω

(c) Calculate the equivalent resistance of the combined resistance found in part (b) and the parallel $3.00 \, \Omega$ resistor.

 Ω

(d) Combine the equivalent resistance found in part (c) with the R_2 resistor.

 Ω

(e) Calculate the total current in the circuit.

 A

(f) What is the voltage drop across the R_2 resistor?

 V


(g) Subtracting the result of part (f) from the battery voltage, find the voltage across the $3.00 \, \Omega$ resistor.

 V

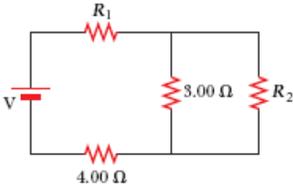(h) Calculate the current in the $3.00 \, \Omega$ resistor.

 A

For parts (a),(b), and (c) use the figure below. (Use the following as necessary: $V = 6.0 \text{ V}$, $R_1 = 5.00 \text{ } \Omega$, and $R_2 = 11.00 \text{ } \Omega$.)



(a) Is it possible to reduce the circuit shown in the figure above to a single equivalent resistor connected across the battery? Explain.

(b) Find the current in the $5.00 \text{ } \Omega$ resistor.

 A

(c) Calculate the power delivered by the battery to the circuit.

 W

Assignment Details

Name (AID): **Homework #3**Submissions Allowed: **5**Category: **Homework**

Code:

Locked: **No**Author: **Segre, Phil** (psegre@physics.emory.edu)

Last Saved:

Permission: **Protected**Randomization: **Person**Which graded: **Last**

Feedback Settings

Before due date

Question Score

Assignment Score

Publish Essay Scores

Question Part Score

Mark

Add Practice Button

Help/Hints

Response

Save Work

After due date

Question Score

Assignment Score

Publish Essay Scores

Key

Question Part Score

Solution

Mark

Add Practice Button

Help/Hints

Response